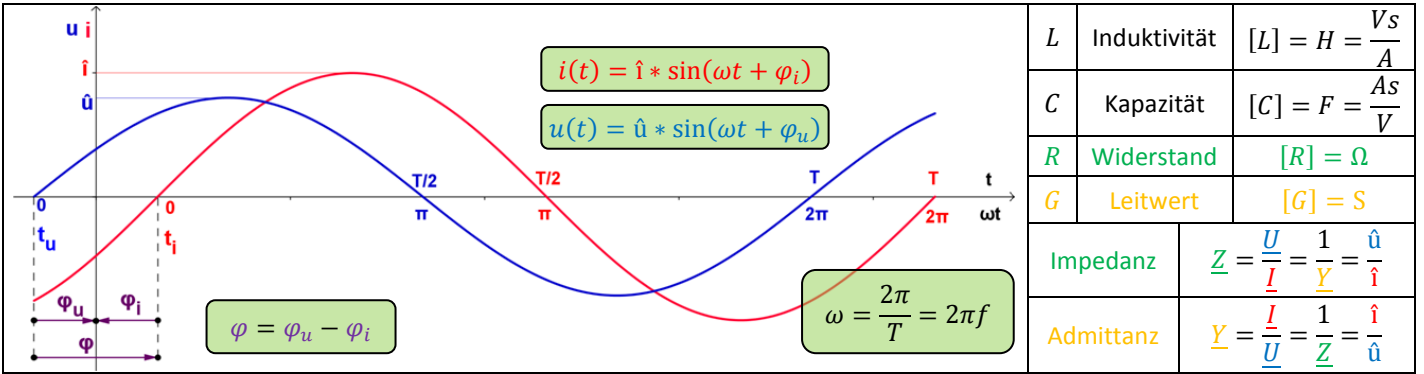


# WECHSELSTROM



Ohmscher Widerstand, R	Ideale Spule, L	Idealer Kondensator, C
$R$ (Widerstand)	$x_L$ (Blindwiderstand) = $\omega L$	$x_C$ (Blindwiderstand) = $\frac{-1}{\omega C}$
$G$ (Leitwert) = $1/R$	$B_L$ (Blindleitwert) = $-1/\omega L$	$B_C$ (Blindleitwert) = $\omega C$
$B = 0$ (ohmisch) = $1/x$	$B < 0$ (induktiv)	$B > 0$ (kapazitiv)
$u(t) = \hat{u} * \sin(\omega t)$ $i(t) = \hat{i} * \sin(\omega t)$	$u(t) = \hat{u} * \sin(\omega t + \varphi_u)$ $i(t) = \hat{i} * \sin(\omega t)$	$u(t) = \hat{u} * \sin(\omega t)$ $i(t) = \hat{i} * \sin(\omega t + \varphi_i)$
$u(t) = R * i(t)$	$u(t) = L * \frac{di(t)}{dt}$	$i(t) = C * \frac{du(t)}{dt}$
$\hat{u} = R * \hat{i}$ $\underline{U} = R * \underline{I}$	$\hat{u} = \omega L * \hat{i}$ $\underline{U} = \omega L * \underline{I}$	$\hat{u} = \frac{1}{\omega C} * \hat{i}$ $\underline{U} = \frac{1}{\omega C} * \underline{I}$
$\varphi_u = \varphi_i$ $\varphi = 0$	$\varphi = \varphi_u - \varphi_i = \frac{\pi}{2}$	$\varphi_u - \varphi_i = -\frac{\pi}{2}$
$\underline{u}(t) = \hat{u} * e^{j\omega t}$	$\underline{u}(t) = L * \frac{d\underline{i}(t)}{dt}$	$\underline{u}(t) = \hat{u} * e^{j\omega t}$
$\underline{Z} = R = \frac{1}{G}$ $\underline{Y} = G = \frac{1}{R}$	$\underline{Z} = jx_L = j\omega L$ $\underline{Y} = jB_L = -\frac{j}{\omega L}$	$\underline{Z} = jx_C = -j\frac{1}{\omega C}$ $\underline{Y} = jB_C = j\omega C$

	Reihenschaltung / Serienschaltung		Parallelschaltung	
Vergleich	$\underline{Z}_1 = \underline{Z}_2$		$\underline{Y}_1 = \underline{Y}_2$	
	<b>R + L</b>	<b>R + C</b>	<b>R + L</b>	<b>R + C</b>
Zeigerdiagramm der Spannung der Ströme				
	$\underline{u} = \underline{u}_R + \underline{u}_L + \underline{u}_C$		$\underline{i} = \underline{i}_R + \underline{i}_L + \underline{i}_C$	
Widerstands-dreieck				
Leitwert-dreieck	$\underline{Z} = R + j\omega L - j\frac{1}{\omega C}$		$\underline{Y} = G - j\frac{1}{\omega L} + j\omega C$	